
# STEDD CHALLENGE TASK

# **Electric Circuits**

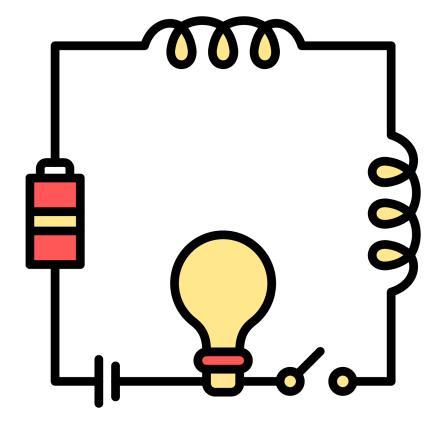

Name:

### **Definition:**

An electric circuit is a path for electricity to flow. It's made of wires connected to a power source, like a battery, and things that use electricity. When the circuit is complete, electricity can travel through it.

### **Challenge:**

Create simple electrical circuits using batteries, wires, and light bulbs or buzzers. Experiment with different circuit configurations to understand how electricity flows and circuits function, learning about conductivity, switches, and circuit diagrams.

### **Brainstorm:**


Materia	ls:			
Labelled	l Diagran	n:		

Method:	Method:				

Test Res	ults:			
Suggeste	ed Impro	vements	:	
Rating:				
		_/_		

# STEDD CHALLENGE TASK

**Electric Circuits** 

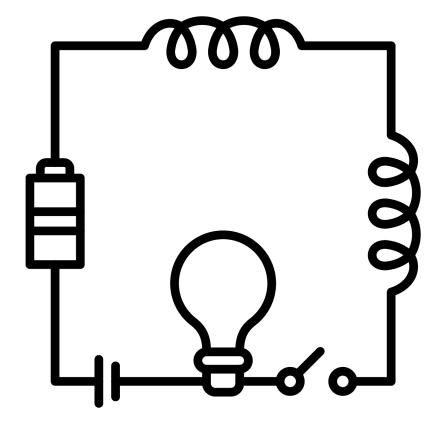

Name:

### **Definition:**

An electric circuit is a path for electricity to flow. It's made of wires connected to a power source, like a battery, and things that use electricity. When the circuit is complete, electricity can travel through it.

### **Challenge:**

Create simple electrical circuits using batteries, wires, and light bulbs or buzzers. Experiment with different circuit configurations to understand how electricity flows and circuits function, learning about conductivity, switches, and circuit diagrams.

### **Brainstorm:**

Materi	<b>als:</b>		
Labelle	d Diagram:	•	

Method:				

Test Re	Test Results:				
Sugges	ted Improve	ements:			